

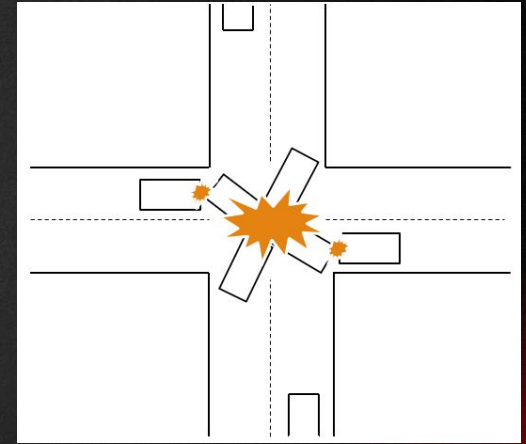


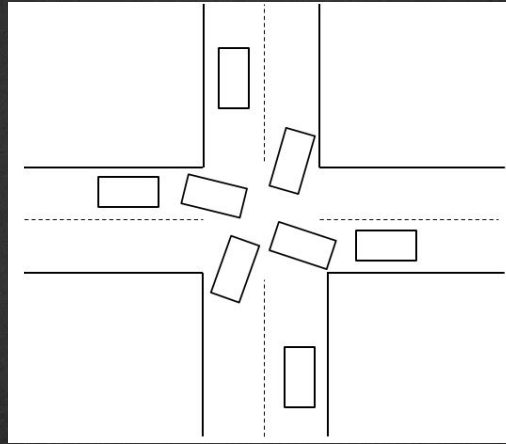



TRAFFIC LIGHT CONTROLLER

EEL2020 DIGITAL DESIGN COURSE PROJECT

PROBLEM STATEMENT

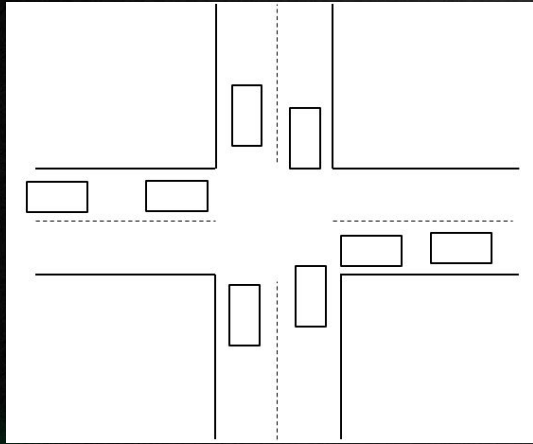


SOLUTION

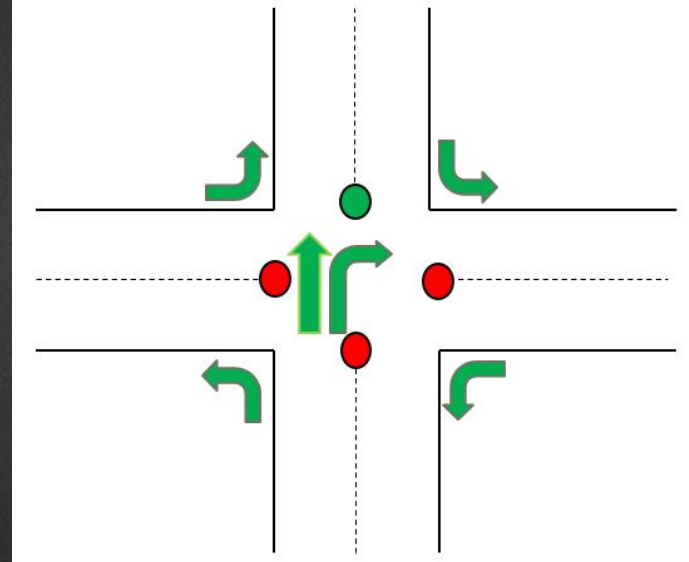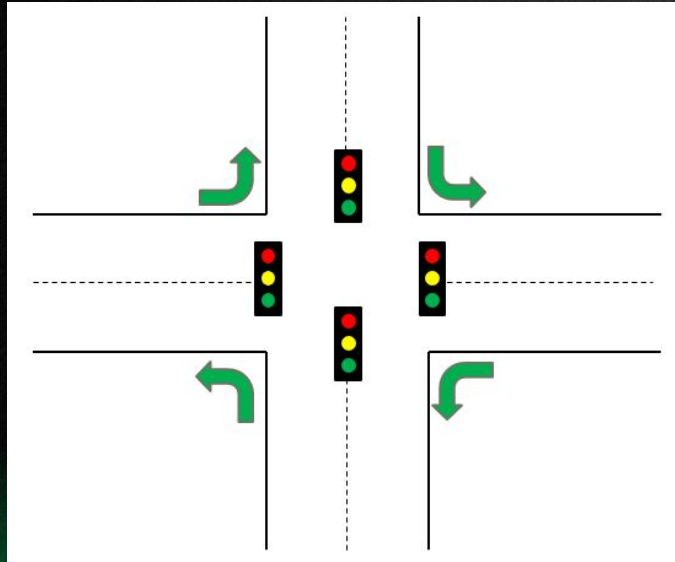




STATE DIAGRAM

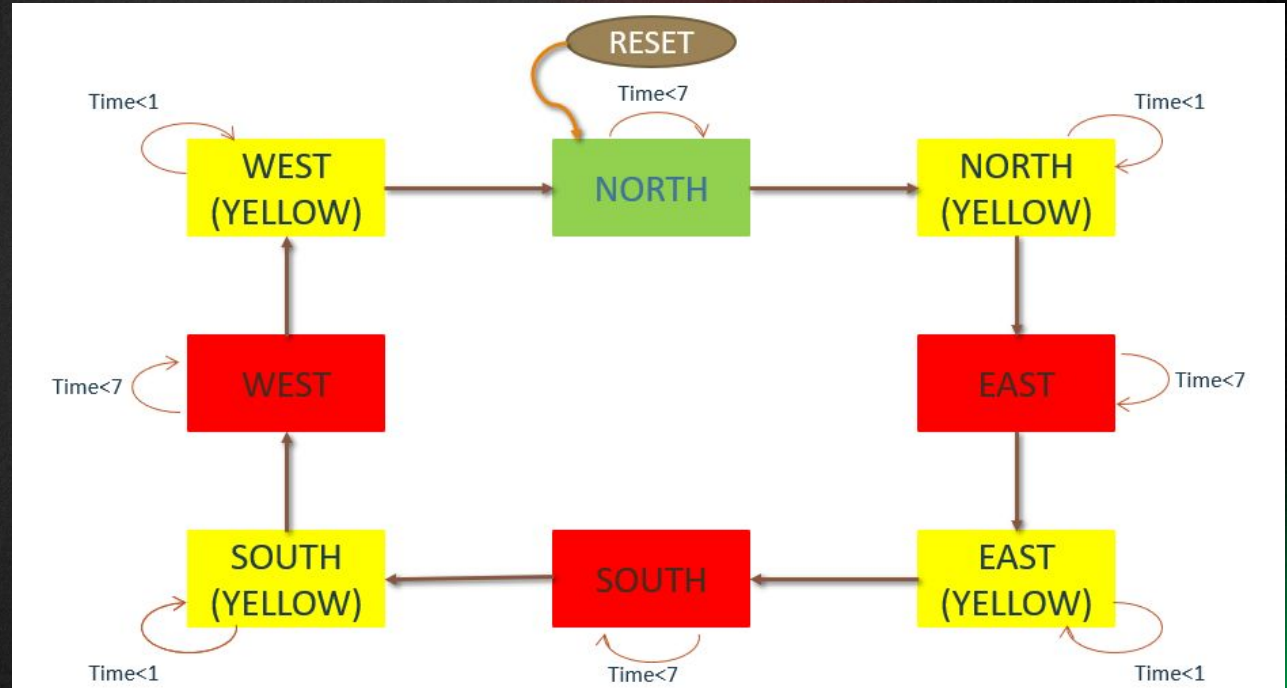

CIRCUIT DIAGRAM

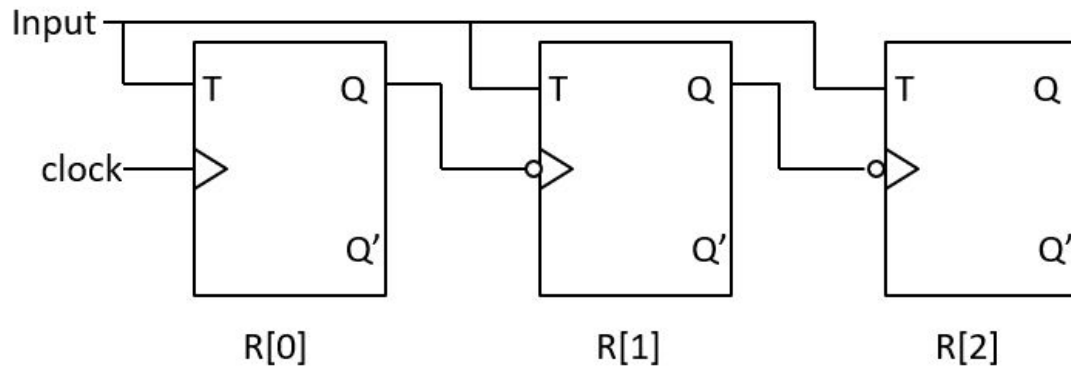

Register


T Flip-Flop:

Characteristics Equation- $T \otimes Q$

For Input=1 , $1 \otimes Q = Q'$
Acts as Counter

For Input=0 , $0 \otimes Q = Q$
Acts as Memory element

CIRCUIT DIAGRAM

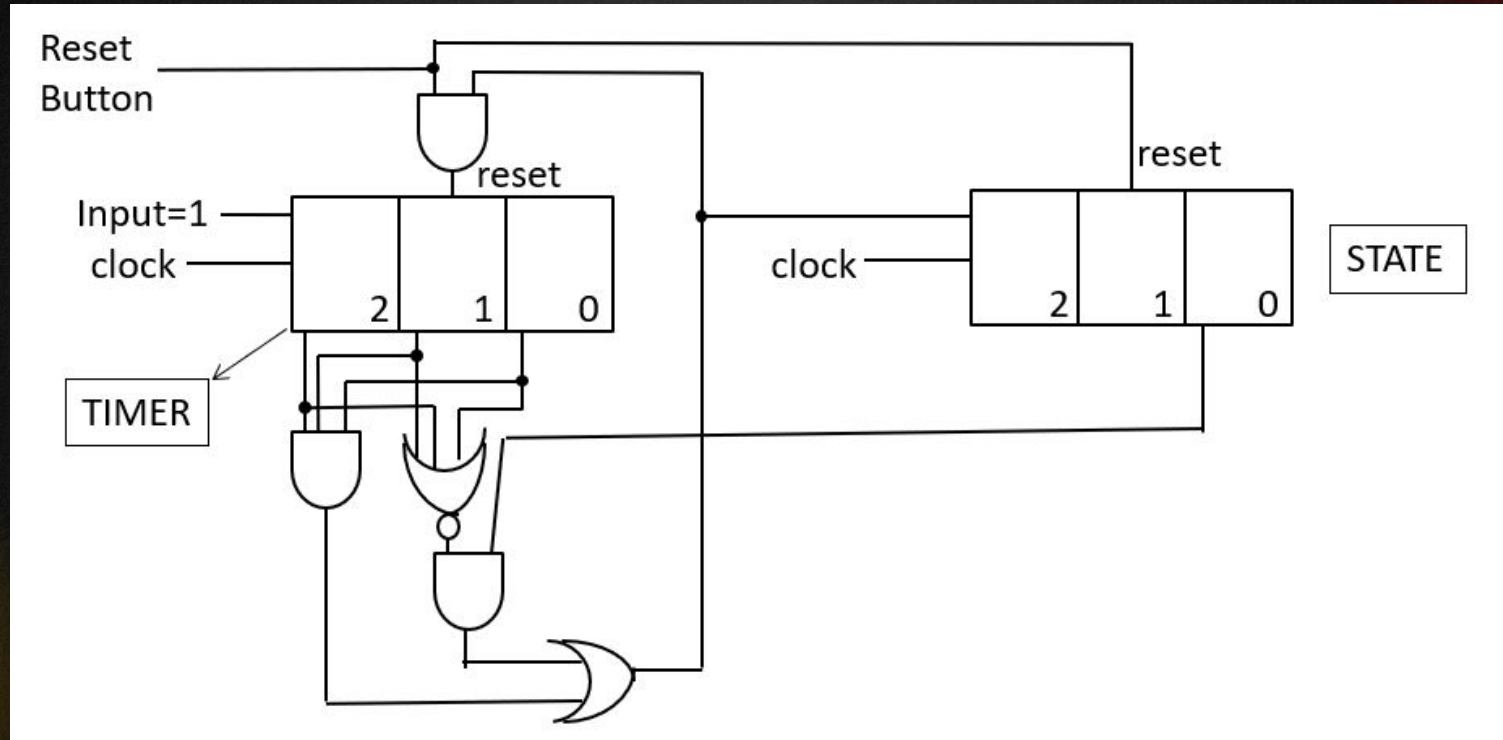

TRUTH TABLE FOR LIGHTS

STATE	S[2]	S[1]	S[0]	NORTH			SOUTH			EAST			WEST		
				G	Y	R	G	Y	R	G	Y	R	G	Y	R
North	0	0	0	1	0	0	0	0	1	0	0	1	0	0	1
North Yellow	0	0	1	0	1	0	0	0	1	0	0	1	0	0	1
South	0	1	0	0	0	1	1	0	0	0	0	1	0	0	1
South Yellow	0	1	1	0	0	1	0	1	0	0	0	1	0	0	1
East	1	0	0	0	0	1	0	0	1	1	0	0	0	0	1
East Yellow	1	0	1	0	0	1	0	0	1	0	1	0	0	0	1
West	1	1	0	0	0	1	0	0	1	0	0	1	1	0	0
West Yellow	1	1	1	0	0	1	0	0	1	0	0	1	0	1	0

LOGIC EQUATIONS

- $NG = S0' \& S1' \& S2'$
- $NY = S0 \& S1' \& S2'$
- $NR = (NG + NY)'$


- $EG = S0' \& S1' \& S2$
- $EY = S0 \& S1' \& S2$
- $ER = (EG + EY)'$




- $SG = S0' \& S1 \& S2'$
- $SY = S0 \& S1 \& S2'$
- $SR = (SG + SY)'$

- $WG = S0' \& S1 \& S2$
- $WY = S0 \& S1 \& S2$
- $WR = (WG + WY)'$

REQUIREMENTS

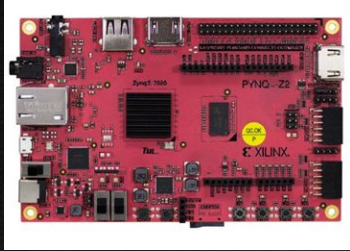


PYNQ-Z2
BOARD

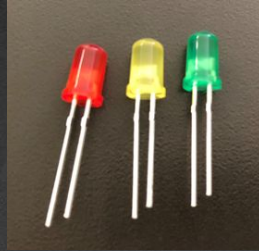


LEDs



RESISTORS

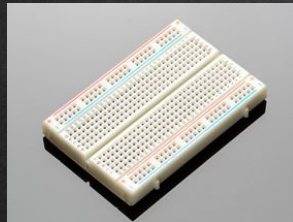

BREADBOARD

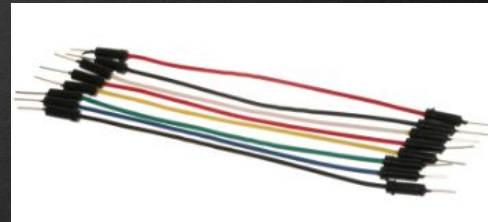

WIRES

IMPLEMENTATION ON BOARD

